

HF Transceiver 101

- what's inside my radio?



Adam Farson VA7OJ

# What is a transceiver?



- A **transceiver** is a transmitter-receiver combination in which the transmit and receive functions share one or more common elements.
- One or more system components (subsystems) are used both for transmitting and for receiving.
- With careful design, this is achievable without compromising transmitter or receiver performance.
- Modern transceivers are based on superheterodyne (*superhet*) architecture.


# *A brief history*



- Prior to the advent of SSB in the mid-1950's, an amateur HF station generally used “separates”:
  - ◆ A superhet receiver, usually single-conversion with 455 kHz IF.
  - ◆ An AM/CW transmitter consisting of a crystal oscillator or VFO, buffer/multipliers, driver, PA and modulator.
- The receiver and transmitter had no common subsystems other than the transmit/receive (T/R) relay and possibly an antenna tuner.
- Acceptance of the heterodyne SSB exciter with crystal or mechanical filters (a superhet in reverse) drove research into sharing RX and TX subsystems.
- Hence, the SSB transceiver was born (1957)
  - ◆ First commercial transceivers: Hallicrafters FPM-200, Collins KWM-1.


# AM vs. SSB:

*"Kilowatts from Heaven"*

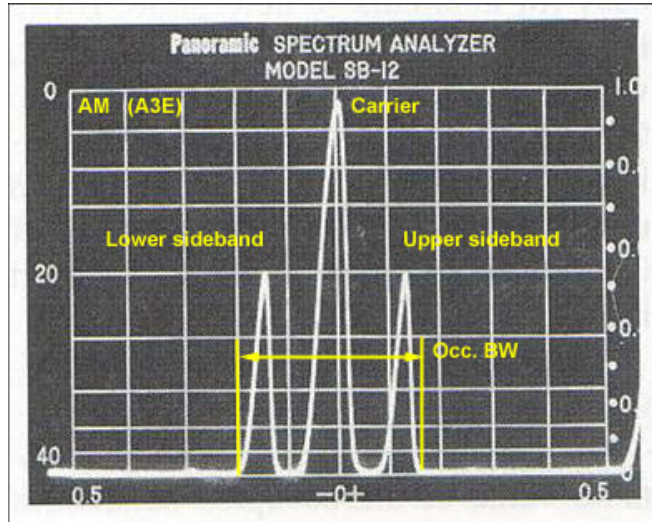
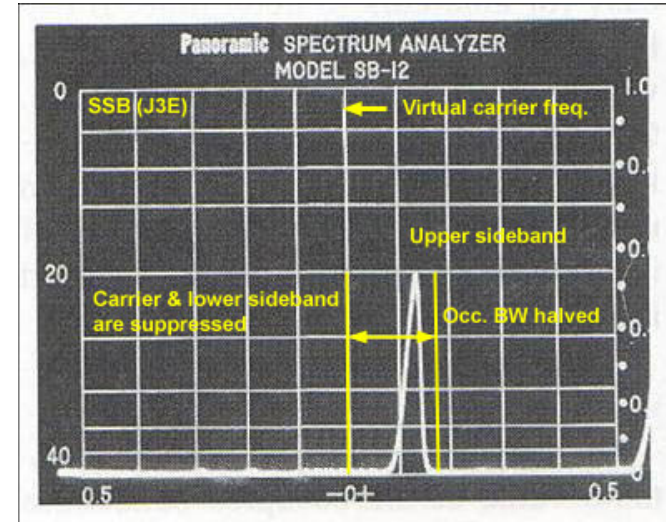
## 100W (PEP) AM signal:

- ◆ 50W in carrier
- ◆ 25W in upper sideband
- ◆ 25W in lower sideband
- ◆ 6 kHz occupied bandwidth (typical)
- ◆ 25% of transmitter power carries unique intelligence



## 100W (PEP) SSB signal (USB):


- ◆ **100W in upper sideband**
- ◆ Carrier & lower sideband suppressed
- ◆ 3 kHz occupied bandwidth (typical)
- ◆ 100% of transmitter output carries unique intelligence
- ◆ S/N improvement: 6 dB for 4X increase in sideband power + 3 dB for 50% less BW = **9 dB total**

# AM Transmitter
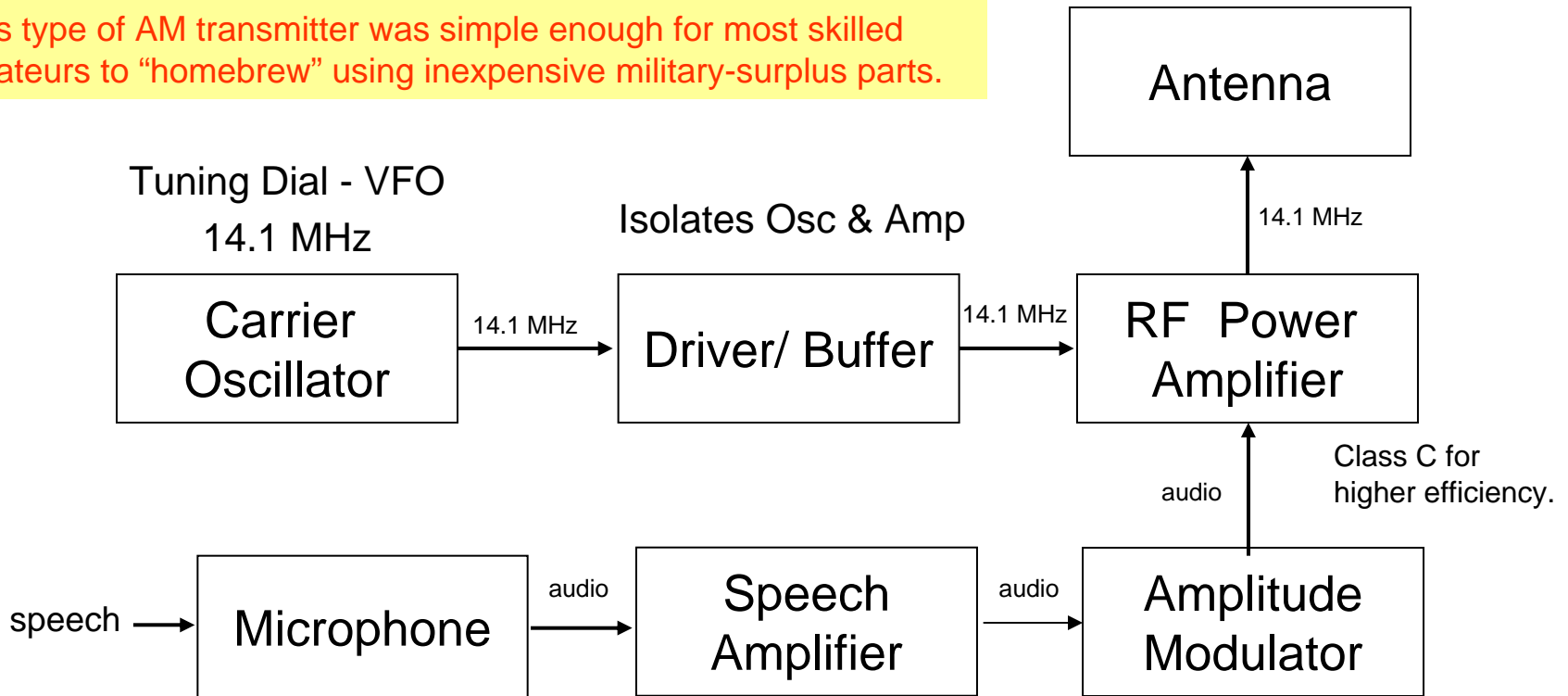
## simplified block diagram



This type of AM transmitter was simple enough for most skilled amateurs to “homebrew” using inexpensive military-surplus parts.




# SSB Transmitter
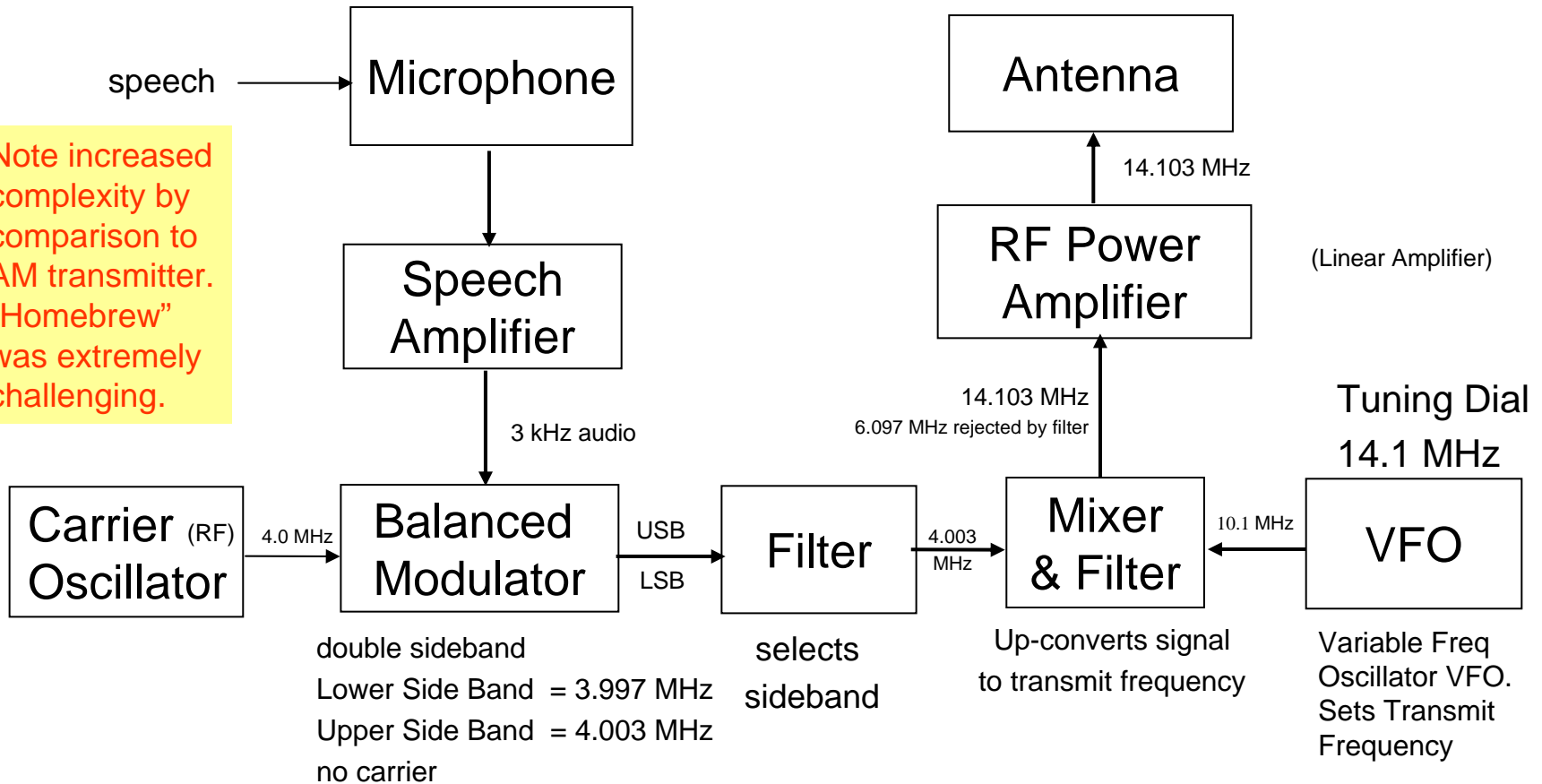
## simplified block diagram



Note increased complexity by comparison to AM transmitter. "Homebrew" was extremely challenging.



# 1960's "Separates"



Hallicrafters SX-115 Receiver 1961 - 64



Hallicrafters HT-37 Transmitter 1960 – 64  
Courtesy Rigpix

- Early amateur SSB stations featured separate receivers and transmitters.
- The transmitter's antenna relay switched the antenna between RX and TX, and muted the receiver on transmit.
- Many transmitter-receiver pairs allowed one-knob "transceive" operation by tuning both the receiver and transmitter with the RX or TX VFO.


# The Collins KWM-1 (1957)



- The Collins KWM-1 was one of the first true SSB/CW transceivers.
- It was introduced in 1957, and cost USD 820 at the time.
- The Collins PTO (permeability-tuned oscillator), developed during WW2, assured good frequency stability for SSB and CW.
- The KWM-1 covered the 20, 15 and 10m bands. It employed 22 tubes (2 x 6146 in PA). Its RF power output was approx. 90W.


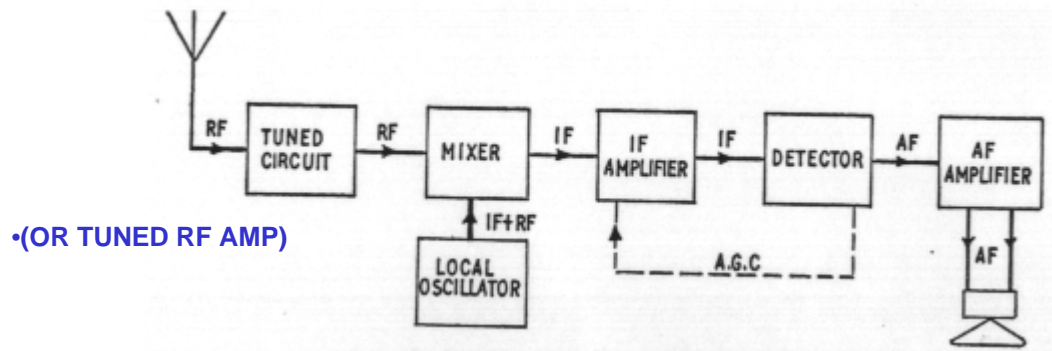
# Simple Superhet Receiver: frequency relationships




- **Example:** RF = 1800 ~ 2000 kHz (tunable); IF = 455 kHz.
- Tracking (ganged) RF and LO tuning.
- Alternative: RF bandpass filter (BW = tuning range for specific band).
- Local Oscillator (LO) = RF + IF = 2255 ~ 2455 kHz. (high-side injection).
- Alternative: RF - IF = 1345 ~ 1545 kHz (low-side injection).
- Bandpass IF amplifier has sufficient BW for mode in use (e.g. AM: 6 kHz).
- AGC (automatic gain control) holds output constant over wide range of RF signal strengths.

# The Superhet Receiver: the problem of images




- Per Slide 9,  $f_1 = 2255$  kHz (LO),  $f_2 = 1800$  kHz (RF);  $(f_1 - f_2) = 455$  kHz (IF).
- If  $f_1 = 2255$  kHz (LO),  $f_2 = 2710$  kHz (RF),  $(f_2 - f_1) = 455$  kHz. Thus, 2710 kHz signal will pass through the IF amplifier and be demodulated. This undesired response is termed the **image**, and is offset from the desired response by **twice the IF**.
- BW of RF amplifier with single-tuned input & output circuits is narrow enough to provide adequate image rejection at frequencies below 10 MHz. (Typical BW = 300 kHz at -3 dB).
- Above 10 MHz, cascaded RF amplifiers with 3 or more tuned circuits are required for acceptable image rejection. Higher IF also improves image rejection, but narrow IF BW is more difficult to obtain at higher freq.
- RF tuned circuits with narrower BW have higher **insertion loss**. This degrades sensitivity. Cascaded RF amplifiers offset this loss, but are more prone to **overload**.
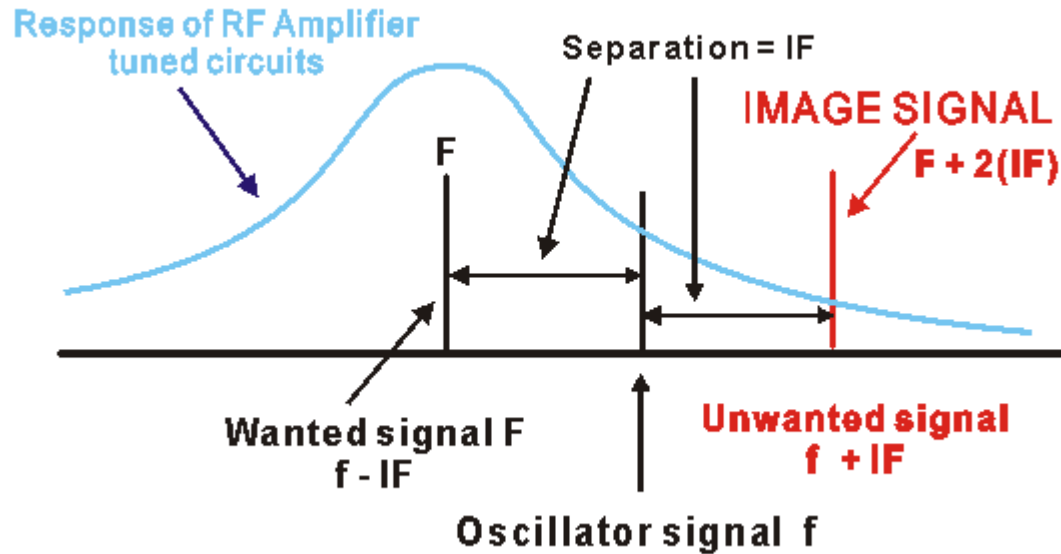
# The Superhet Receiver: the problem of images



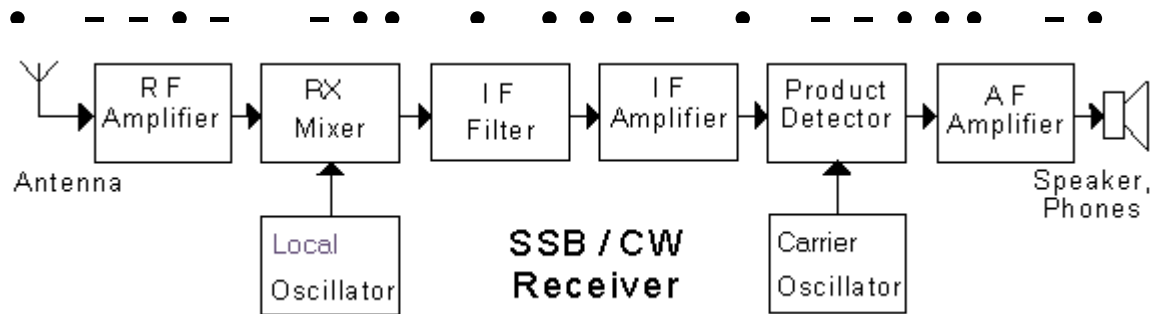
# Basic SSB/CW Superhet Receiver (20m USB)




- Example 1: RF signal is 14100 kHz USB (suppressed carrier frequency).
- Actual USB signal typically occupies 14000.3 ~ 14002.4 kHz.
- IF = 9000 kHz. IF filter BW = 2.4 kHz. IF signal is 9000.3 ~ 9002.4 kHz.
- Local oscillator (LO) tuned to  $(14100 - 9000) = 5100$  kHz.
- LO tunes 5000 – 5350 kHz to cover entire 20m band (14000 ~ 14350 kHz).
- Carrier oscillator set at 9000 kHz (at -20 dB point on filter skirt, for best suppression of opposite sideband and carrier).
- Product detector mixes 9000.3 ~ 9002.4 kHz IF with 9000 kHz carrier oscillator output to yield audio output, 300 Hz ~ 2.4 kHz.
- Image frequency is  $(9000 - 5100) = 3900$  kHz. 20m bandpass filter at RF amplifier input suppresses image response.
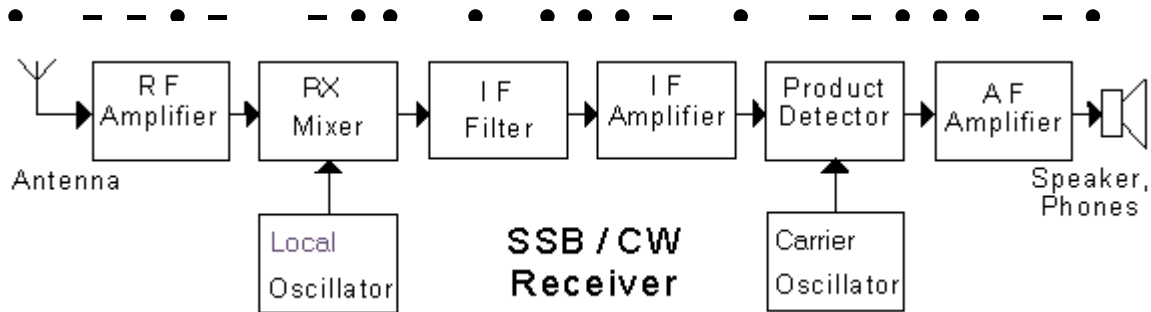
# Basic SSB/CW Superhet Receiver (80m LSB)



- Example 2: RF signal is 3600 kHz LSB (suppressed carrier frequency).
- Actual LSB signal typically occupies 3597.6 ~ 3599.7 kHz.
- IF = 9000 kHz. IF filter BW = 2.4 kHz. IF signal is 8997.6 ~ 8999.7 kHz.
- Local oscillator (LO) tuned to  $(9000 - 3600) = 5400$  kHz.
- LO tunes 5500 – 5000 kHz to cover entire 80m band (3500 ~ 4000 kHz).
- **80m and 20m bands use same LO tuning range.**
- Carrier oscillator set at 9000 kHz (at -20 dB point on filter skirt, for best suppression of opposite sideband and carrier).
- Product detector mixes 8997.6 ~ 8999.7 kHz IF with 9000 kHz carrier oscillator output to yield audio output, 300 Hz ~ 2.4 kHz.


# Now let's add the transmitter section!

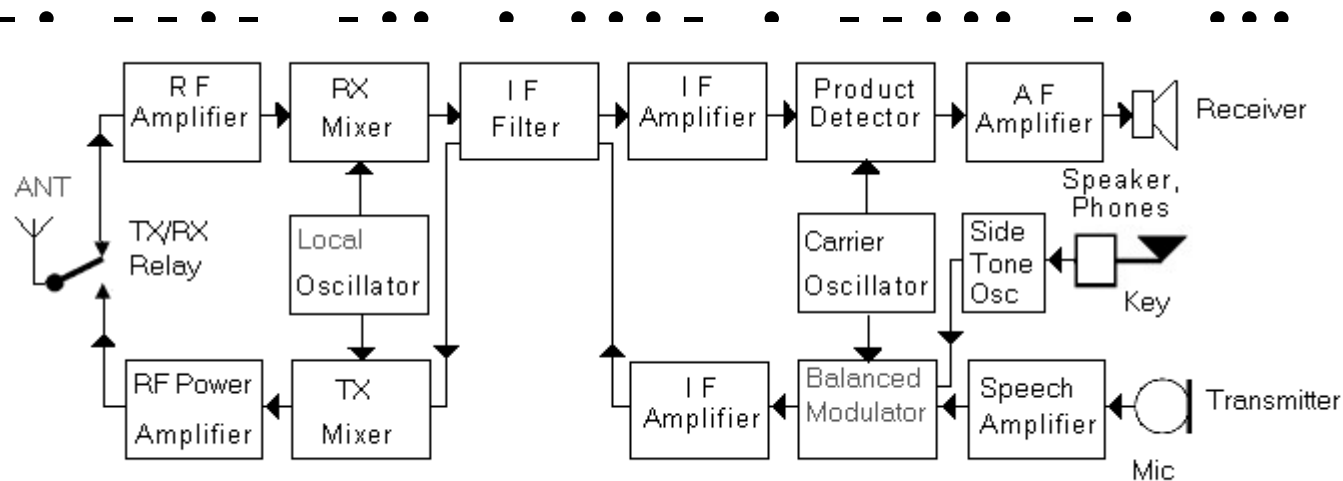

**SSB-CW Transceiver**

- Carrier oscillator, IF filter and local oscillator are shared between receiver and transmitter.
- Carrier oscillator feeds 9000 kHz carrier to Balanced Modulator.
- Mic audio is amplified and mixed with carrier to yield USB 9000.3 ~ 9002.4 kHz and LSB (8997.6 ~ 8999.7 kHz). IF Filter passes USB and suppresses LSB.
- Local oscillator tuned to  $(14100 - 9000) = 5100$  kHz.
- TX mixer mixes IF with local oscillator output to yield USB TX signal (14000.3 – 14002.4 kHz).
- RF power amplifier raises TX signal power to 100W (typical).
- TX/RX relay routes antenna to RX input or TX output as required.


# CW Operation

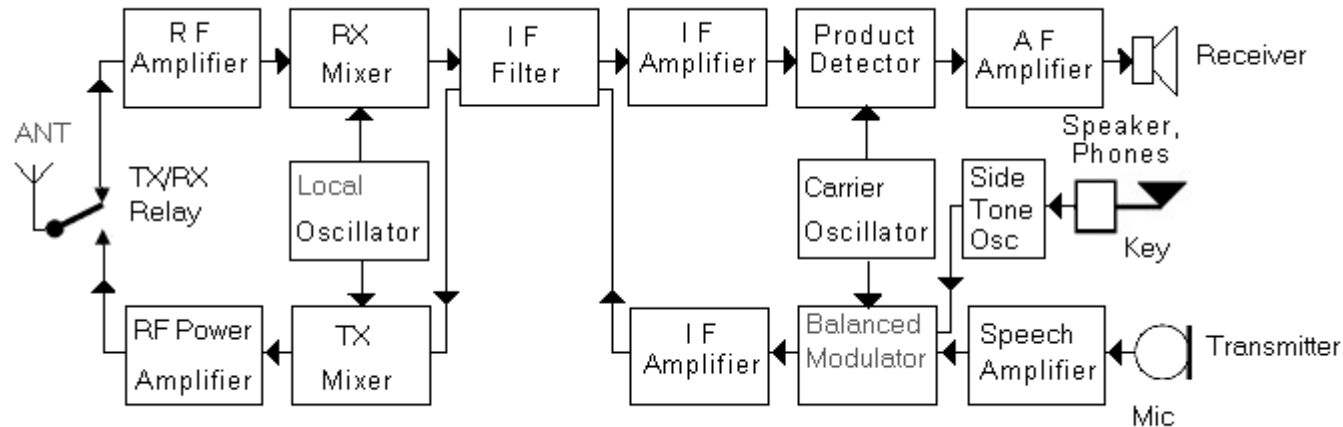

**SSB-CW Transceiver**

- CW IF filter is narrower than for SSB (usually 500 or 250 Hz). Centre frequency is 9000 kHz.
- Example: 500 Hz IF filter. Signal is at 14010 kHz. Local oscillator at 5009.650 kHz yields IF at 9000.350 kHz (-20 dB point on upper filter skirt).
- Carrier oscillator at 8999.650 kHz yields 700 Hz CW pitch at audio output.
- When transmitting, sidetone oscillator is keyed and feeds 700 Hz tone to balanced modulator. This is mixed with 8999.650 Hz carrier to produce 9000.350 kHz IF.
- Transmit mixer mixes this IF with 5009.650 kHz local oscillator output to yield 14010 kHz RF signal which is amplified to 100W and transmitted as for SSB.

# AGC and ALC

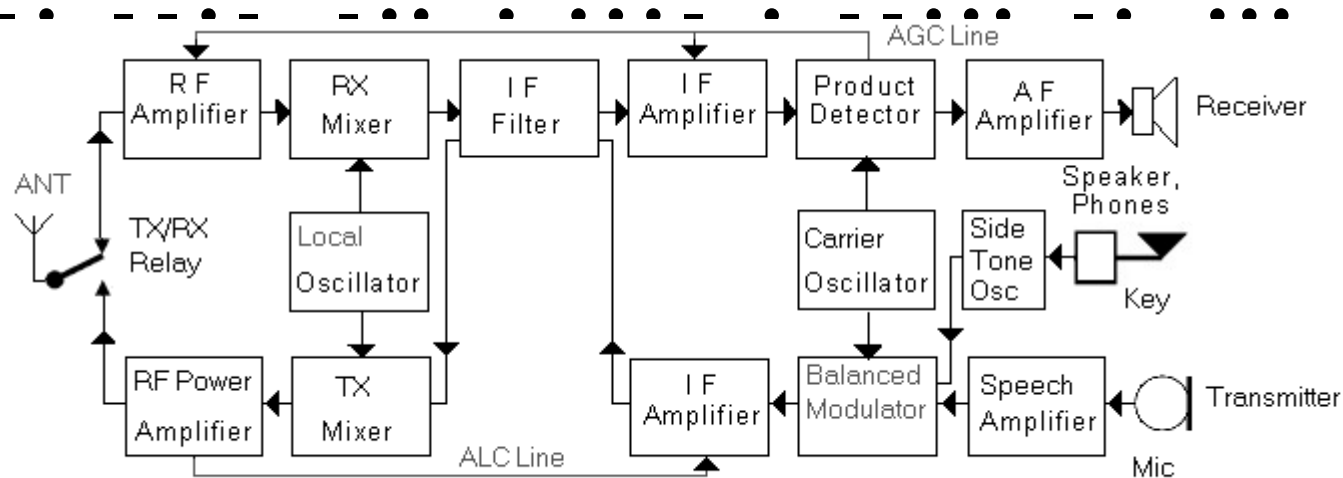


**SSB-CW Transceiver**

- **Receiver AGC (automatic gain control):** An AGC detector samples the average audio or IF output signal level, and feeds it back to the RF and/or IF stages to hold the gain constant over a range of input signal levels. The AGC line also drives the S-meter.
- **Transmitter ALC (automatic level control):** A reflectometer samples the **forward** and **reflected** power at the output of the RF power amplifier, and feeds it back to the transmit IF amplifier to **level the transmitter output at a preset value** and **protect the transmitter against damage due to load mismatch**.



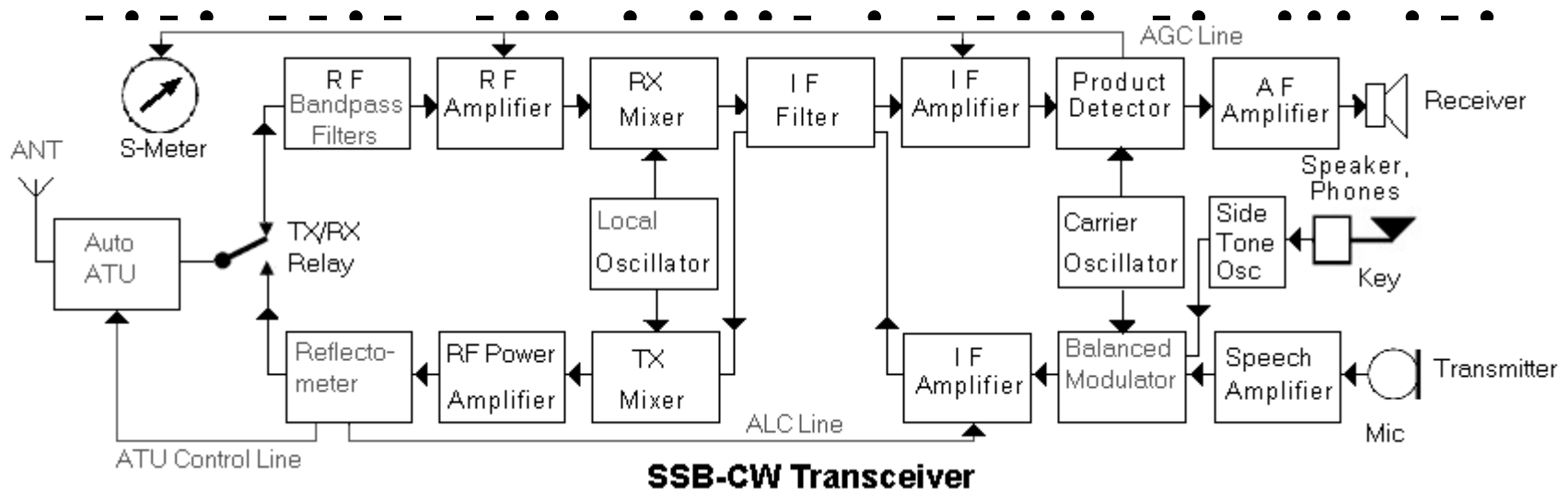
# Auto Antenna Tuner and RF Bandpass Filters



- **Automatic Antenna Tuner (Auto ATU):** A T-network (series C – shunt L – series C) located between the antenna socket and the TX/RX relay. It can be switched out of signal path if desired.
- Auto ATU matches complex antenna impedance to the 50Ω load required by the transmitter. It will also provide near optimum noise matching for the receiver.
- Auto ATU is controlled by reflected-power signal from reflectometer in transmitter.
- **RF Bandpass Filters (preselector filters)** suppress image response, and protect receiver RF amplifier (preamp) against overload by strong out-of-band signals.




# RF Gain & Attenuator

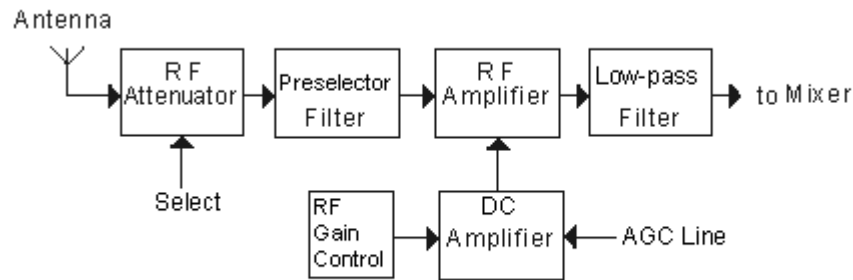

**Gain-Controlled RF Amplifier with Front-End RF Attenuator**

- **RF front-end attenuator** located between antenna input and preselector filter.
- 6, 12 or 18 dB attenuation (typ.) selected by front-panel control.
- **RF Gain control** increases AGC bias on gain-controlled RF amplifier (and/or 1<sup>st</sup> IF amplifier in some designs); raises AGC threshold.
- Receiver dynamic range increases by amount of attenuation inserted.
- Usually, band noise is 10 to 12 dB above Rx noise floor; attenuation does not significantly degrade noise figure. Attenuator & RF Gain can be used together.



# Noise Blanker (pulse-gate type)

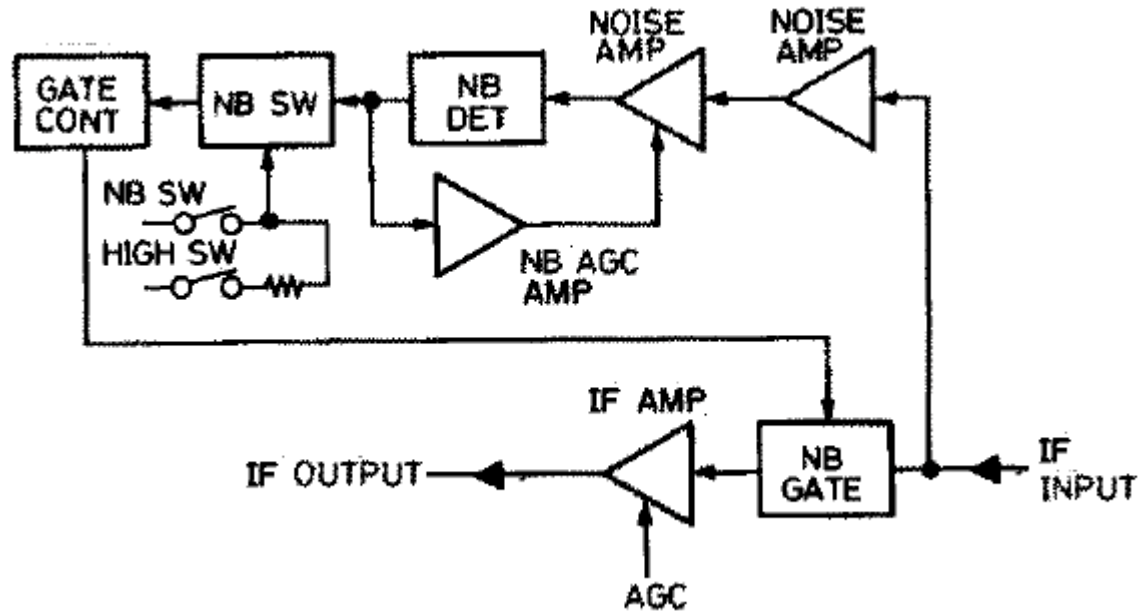

- A portion of IF signal is amplified by **NOISE AMP**, detected by **NB DET** and applied to **NB SW**. **HIGH SW** switch increases **NB SW** threshold.
- When detected noise voltage exceeds **NB SW** threshold, **NB SW** sends transition to **GATE CONT** to close **NB GATE** & break IF signal path for duration of noise pulse.
- **NB AGC** loop time constant holds average signal level at **NB DET** constant, but is too long to respond to impulse noise.

# Compressor


(transmit speech processor)

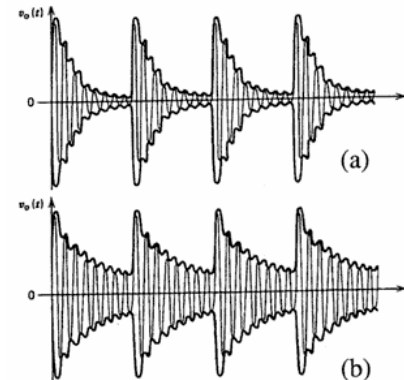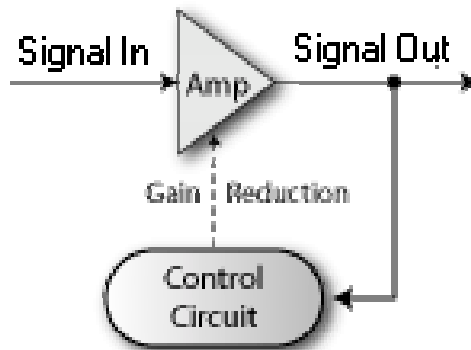

SSB waveforms: (a) unprocessed speech (the repeated word "three") with 16dB peak-to-average ratio; (b) the same word with 6dB of compression

- Compressor is a gain-controlled amplifier driving an envelope detector with an integrator. The detector output controls the amplifier gain and holds output level constant over a wide input level range. Typically, the compressor is in the TX IF signal path and acts on the TX IF amplifier.
- Compressor decreases peak/average ratio of SSB signal, increasing average power output ("talk power").
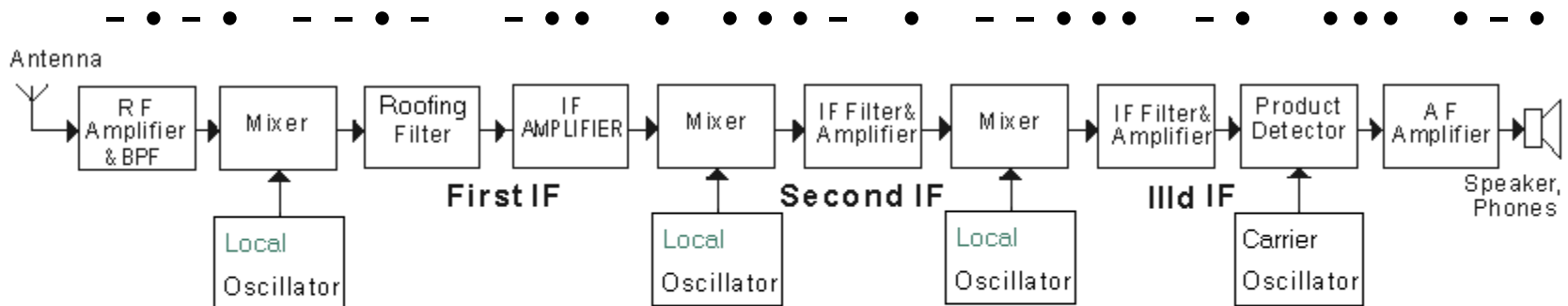
# Triple-Conversion General-Coverage Transceiver RX Section (up-converting)



- **Typical frequency coverage:** 0.5 ~ 30 MHz. 1<sup>st</sup> IF > 30 MHz (typ. 45~ 70 MHz).
- Each RF amplifier BPF covers ½ octave, e.g. 6 ~ 9, 9 ~ 13.5 MHz. Approx. 12 BPFs required for complete range. Image rejection is high, as image freq. >> 30 MHz.
- **1<sup>st</sup> LO in VHF range.** For 70 MHz 1<sup>st</sup> IF, 1<sup>st</sup> LO covers 70.5 ~ 100.5 MHz.
- 1<sup>st</sup> IF filter is **roofing filter**: BW sufficient to pass widest mode (15 kHz for FM).
- Roofing filter protects IF chain against strong out-of-band signals.
- **Typically:** 2<sup>nd</sup> IF is 9 MHz, 3<sup>rd</sup> IF is 455 kHz.
- **Transmit signal flow:** audio → 455 kHz → 9 MHz → 70 MHz → RF
- Almost all modern HF transceivers employ **up-converting** architecture.
- Many current transceivers have **DSP** (digital signal processing) at the final IF.

# *Links for further study*



- **NSARC Series on HF Receivers**
  - ◆ [Part 1](#)
  - ◆ [Part 2](#)
  - ◆ [Part 3](#)
- **DSP in HF Radios**
  - ◆ [Presentation](#)